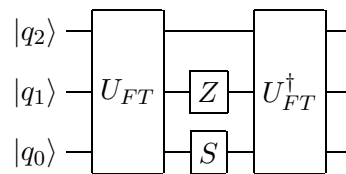


Quantum Computing Epiphany Assignment 4

- Q1** Give the inverse for the Quantum Fourier Transform U_{FT} , and give the explicit quantum circuit for the inverse for three qubits.
- Q2** Consider a 3-qubit system, and consider the unitary transform $U_{FT}^\dagger S_0 Z_1 U_{FT}$, represented by the quantum circuit below.



Show that this circuit implements the operation $x \rightarrow x + 2 \pmod 8$.

- Q3** Find the period of the function $f(a) = y^a \pmod N$ for $N = 713$, for some y of your choosing. (I recommend using a computer for doing the exponentials and modular operations involved in finding the period.) If the period is odd, choose again. Use the result to find a prime factor of N .